

# Laboratory Exercise 1

## Switches, Lights, and Multiplexers

The purpose of this exercise is to learn how to connect simple input and output devices to an FPGA chip and implement a circuit that uses these devices. We will use the switches  $SW_{15-0}$  on the BASYS3 board as inputs to the circuit. We will use light emitting diodes (LEDs) and 7-segment displays as output devices.

### Part I

The BASYS3 board provides 16 toggle switches, called  $SW_{15-0}$ , that can be used as inputs to a circuit, and 18 red lights, called  $LEDR_{17-0}$ , that can be used to display output values. Figure 1 shows a simple Verilog module that uses these switches and shows their states on the LEDs. Since there are 16 switches and lights it is convenient to represent them as vectors in the Verilog code, as shown. We have used a single assignment statement for all 16  $LEDR$  outputs, which is equivalent to the individual assignments

```
assign LEDR[15] = SW[15];  
assign LEDR[14] = SW[14];  
assign LEDR[0] = SW[0];
```

The BASYS3 board has hardwired connections between its FPGA chip and the switches and lights. To use  $SW_{17-0}$  and  $LEDR_{17-0}$  it is necessary to include in your Vivado project the correct pin assignments, which are given in the *BASYS3 User Manual*. For example, the manual specifies that  $SW_0$  is connected to the FPGA pin  $N25$  and  $LEDR_0$  is connected to pin  $AE23$ . A good way to make the required pin assignments is to import into the software the file called *BASYS3 pin assignments.csv*, which is provided on the *BASYS3 System CD* and in the University Program section of Altera's web site. The procedure for making pin assignments is described in the tutorial *Vivado Introduction using Verilog Design*, which is also available from Xilinx.

The file uses the names  $SW[0] \dots SW[17]$  and  $LEDR[0] \dots LEDR[17]$  for the switches and lights, which is the reason we used these names in Figure 1.

```
// Simple module that connects the SW switches to the LEDR lights  
module part1 (SW, LEDR);  
  
    input [17:0] SW;    // toggle switches  
    output [17:0] LEDR; // red LEDs  
  
    assign LEDR = SW;  
endmodule
```

Figure 1. Verilog code that uses the BASYS3 board switches and lights.


Perform the following steps to implement a circuit corresponding to the code in Figure 1 on the BASYS3 board.

1. Create a new Vivado project for your circuit. Select as the target chip, which is the FPGA chip on the Xilinx board.
2. Create a Verilog module for the code in Figure 1 and include it in your project.

3. Include in your project the required pin assignments for the BASYS3 board, as discussed above. Compile the project.
4. Download the compiled circuit into the FPGA chip. Test the functionality of the circuit by toggling the switches and observing the LEDs.

## Part II


Figure 2a shows a sum-of-products circuit that implements a 2-to-1 *multiplexer* with a select input  $s$ . If  $s = 0$  the multiplexer's output  $m$  is equal to the input  $x$ , and if  $s = 1$  the output is equal to  $y$ . Part b of the figure gives a truth table for this multiplexer, and part c shows its circuit symbol.

 

a) Circuit

$s$	$m$
0	$x$
1	$y$

b) Truth table

 

c) Symbol

Figure 2. A 2-to-1 multiplexer.

The multiplexer can be described by the following Verilog statement:

```
assign m = (~s & x) | (s & y);
```

You are to write a Verilog module that includes eight assignment statements like the one shown above to describe the circuit given in Figure 3a. This circuit has two eight-bit inputs,  $X$  and  $Y$ , and produces the eight-bit output  $M$ . If  $s = 0$  then  $M = X$ , while if  $s = 1$  then  $M = Y$ . We refer to this circuit as an eight-bit wide 2-to-1 multiplexer. It has the circuit symbol shown in Figure 3b, in which  $X$ ,  $Y$ , and  $M$  are depicted as eight-bit wires. Perform the steps shown below.

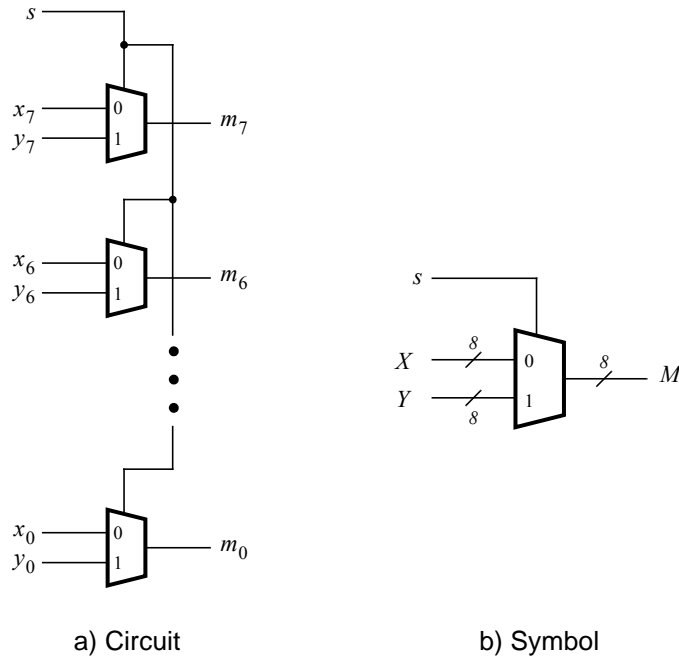



Figure 3. An eight-bit wide 2-to-1 multiplexer.

1. Create a new Vivado project for your circuit.
2. Include your Verilog file for the eight-bit wide 2-to-1 multiplexer in your project. Use switch  $SW_{17}$  on the BASYS3 board as the  $s$  input, switches  $SW_{7-0}$  as the  $X$  input and  $SW_{15-8}$  as the  $Y$  input. Connect the  $SW$  switches to the red lights  $LEDR$  and connect the output  $M$  to the green lights  $LEDG_{7-0}$ .
3. Include in your project the required pin assignments for the BASYS3 board. As discussed in Part I, these assignments ensure that the input ports of your Verilog code will use the pins on the Cyclone II FPGA that are connected to the  $SW$  switches, and the output ports of your Verilog code will use the FPGA pins connected to the  $LEDR$  and  $LEDG$  lights.
4. Compile the project.
5. Download the compiled circuit into the FPGA chip. Test the functionality of the eight-bit wide 2-to-1 multiplexer by toggling the switches and observing the LEDs.
 
### Part III

In Figure 2 we showed a 2-to-1 multiplexer that selects between the two inputs  $x$  and  $y$ . For this part consider a circuit in which the output  $m$  has to be selected from our inputs  $u, v, w, x$ . Part a of Figure 4 shows how we can build the required 4-to-1 multiplexer by using three 2-to-1 multiplexers. The circuit uses a 3-bit select input  $s_2s_1s_0$  and implements the truth table shown in Figure 4b. A circuit symbol for this multiplexer is given in part c of the figure.


Recall from Figure 3 that an eight-bit wide 2-to-1 multiplexer can be built by using eight instances of a 2-to-1 multiplexer. Figure 5 applies this concept to define a two-bit wide 4-to-1 multiplexer. It contains three instances of the circuit in Figure 4a.



a) Circuit

$s_1$	$s_0$	$m$
0	0	$u$
0	1	$v$
1	0	$w$
1	1	$x$

b) Truth table

 

c) Symbol

30E tgcvg" c" pgy "S wct wu" Kk r tqlgev" hqt" { qwt" ekewk" vq" ko r ngo gpv" vj g" 4" dk" y kf g" 6/ vq" 3" O wnr rnzgt "" 40E tgcvg" c" Xgtkqi "gpvk" { hqt" vj g" vj tgg/ dk" y kf g" 6/ vq" 3" o wnr rnzgt 0E qppgev" ku" ugrgev" lpr wu" vq" uy kej gu" UY 38 37. "cpf" "vug" vj g" tgo clpki "35" uy kej gu" UY : 2" vq" r tqxkf g" vj g" hqt" "4/ dk" lpr wu" W" vq" [ 0E qppgev" vj g" UY "uy kej gu" vq" vj g" tgf "NGDR and the output to the green LEDG 50penf g" lp" { qwt" r tqlgev" vj g" tgs vktgf "r lp" cuuki po gpw" eqput clpw" hqt" vj g" DCU U5" dqctf and Eqo r kg" vj g" r tqlgev" 06F qy pmcf " vj g" eqo r kgf "ekewk" lpvq" vj g" HRI C" ej kr 0' 4. Vguv" vj g" hwpev" qpckk" { qh" vj g" vj tgg/ dk" y kf g" 4/ vq" 3" o wnr rnzgt" d{ "vqi i rki "vj g" uy kej gu" cpf "qdugt xkpi "vj g" NGF u0Gpuwt g" vj cv" gcej " qh" vj g" lpr wu" W" vq" [ "ecp" dg" r tqr gtn" { ugrgev" gf "cu" qwr w" O .

## Part IV

Figure 6 shows a 7-segment decoder module that has the three-bit input  $c_2c_1c_0$ . This decoder produces seven outputs that are used to display a character on a 7-segment display. Table 1 lists the characters that should be displayed for each valuation of  $c_2c_1c_0$ . To keep the design simple, only four characters are included in the table .

The seven segments in the display are identified by the indices 0 to 6 shown in the figure. Each segment is illuminated by driving it to the logic value 0. You are to write a Verilog module that implements logic functions that represent circuits needed to activate each of the seven segments. Use only simple Verilog **assign** statements in your code to specify each logic function using a Boolean expression.

 


Figure 6. A 7-segment decoder.

$c_2c_1c_0$	Character
000	F
001	P
010	G
011	A
100	
101	
110	
111	

Table 1. Character codes.

Perform the following steps:

Create a Vivado project for your circuit and implement it in the Xilinx FPGA board to display one of the four characters using a Verilog code

 


Figure 7. A circuit that can select and display one of four characters.

```

module part5 (SW, HEX0);
  input [14:0] SW;      // toggle switches
  output [0:6] HEX0;   // 7-seg displays

  wire [2:0] M;

  mux_2bit_4to1 M0 (SW[16:15], SW[14:12], SW[11:9], SW[8:6], SW[5:3], SW[2:0], M);
  char_7seg H0 (M, HEX0);
endmodule

// implements a 2-bit wide 4-to-1 multiplexer
module mux_2bit_4to1 (S, U, V, W, X);
  input [1:0] S, U, V, W, X;
  output [2:0] M;

  ... code not shown

endmodule

// implements a 7-segment decoder for F, P, G, A
module char_7seg (C, Display);
  input [1:0] C;      // input code
  output [0:6] Display; // output 7-seg code

  ... code not shown

endmodule

```

Figure 8. outline of the Verilog code for the circuit in Figure 7.

Perform the following steps.

1. Create a new Vivado project for your circuit.
2. Include your Verilog module in the Vivado project. Connect the switches  $SW_{16-15}$  to the select inputs of each of the five instances of the three-bit wide 5-to-1 multiplexers. Also connect  $SW_{14-0}$  to each instance of the multiplexers as required to produce the patterns of characters. Connect the outputs of the multiplexers to the 7-segment displays *HEX3*, *HEX2*, *HEX1*, and *HEX0*.
3. Include the required pin assignments as per the constraints .XDC file for the BASYS3 board for all switches, LEDs, and 7-segment displays. Compile the project.
4. Download the compiled circuit into the FPGA chip. Test the functionality of the circuit by setting the proper character codes on the switches  $SW_{14-0}$  and then toggling  $SW_{16-15}$  to observe the rotation of the characters.

